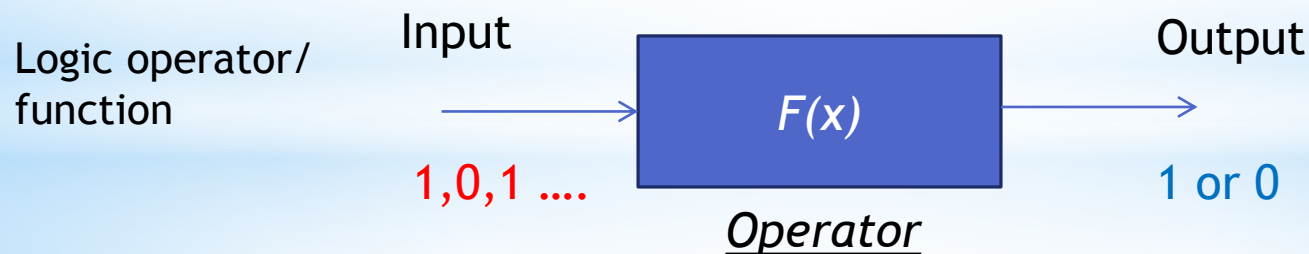
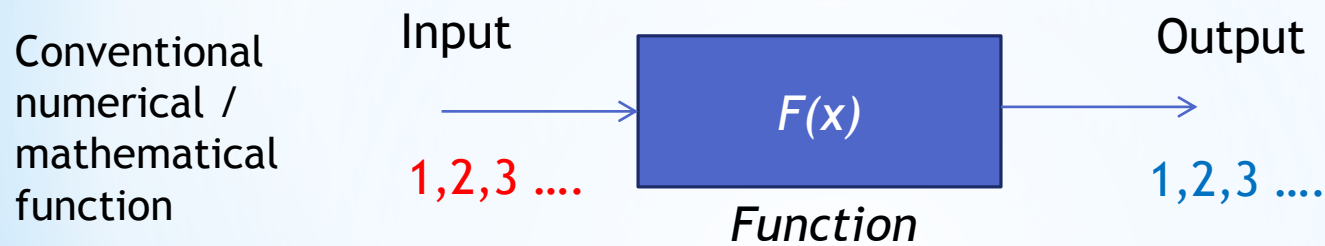


Logic Gates and Boolean Functions

- 3.1 Basic logic gates
- 3.2 Boolean algebra
- 3.3 Logic Circuit and Boolean Expression
- 3.4 Logic function - SOP, POS, minterm,
maxterm, canonical form
- 3.5 Synthesis of logic function
- 3.6 Structure using one gate type

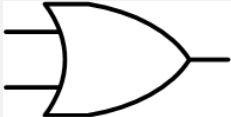

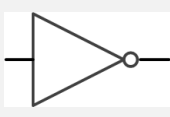
3.1 Basic Logic Gates

- The term **gate** describes a circuit that performs a basic logic operation.



Binary decision output e.g, Yes/No ; True/False and 1/0 .

Logic Operator

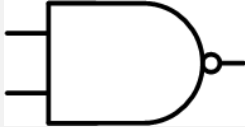

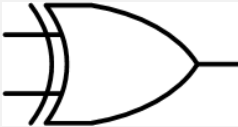
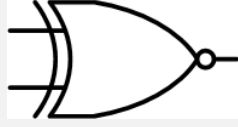
	OR gate	AND gate	NOT gate
Binary/Unary operator ?	Binary	Binary	Unary
Symbols	1: $+$ 2: \vee	1: \cdot 2: \wedge 3: absence of an operator	1: $'$ 2: \sim 3: $-$
Examples	1: $a + b$ 2: $a \vee b$	1: $a \cdot b$ 2: $a \wedge b$ 3: ab	1: a' 2: $\sim a$ 3: \bar{a}
Logic Gate Symbol			

Truth table of OR		
a	b	$a + b$
0	0	0
0	1	1
1	0	1
1	1	1

Truth table of AND	
a b	a b
0 0	0
0 1	0
1 0	0
1 1	1

Truth table of NOT	
a	\bar{a}
0	1
1	0

Logic Operator

Operation	NAND	NOR	XOR	XNOR
a b	$(ab)'$	$(a + b)'$	$a \oplus b$	$\overline{a \oplus b}$
0 0	1	1	0	1
0 1	1	0	1	0
1 0	1	0	1	0
1 1	0	0	0	1
Logic Gate Symbol				

3.2 Boolean Algebra

- A set of element S with at least two different elements (x, y) satisfying binary operations $(+)$ and (\cdot) .
- For Boolean algebra in which $S = \{0, 1\}$, the formulation is referred as switching function.

Basic Postulates

If $x, y \in S$,

$$x + y = y + x$$

$$x \cdot y = y \cdot x$$

commutative

If $x, y, z \in S$,

$$x + (y + z) = (x + y) + z$$

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

associative

If $x, y, z \in S$,

$$x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$x + (y \cdot z) = (x + y) \cdot (x + z)$$

distributive

Distributive Law

- Proof

$$x + y \cdot z = (x + y) \cdot (x + z)$$

$x \ y \ z$	$y \cdot z$	$x + y \cdot z$	$x + y$	$x + z$	$(x + y) \cdot (x + z)$
0 0 0	0	0	0	0	0
0 0 1	0	0	0	1	0
0 1 0	0	0	1	0	0
0 1 1	1	1	1	1	1
1 0 0	0	1	1	1	1
1 0 1	0	1	1	1	1
1 1 0	0	1	1	1	1
1 1 1	1	1	1	1	1

Duality

- If an expression is valid in Boolean algebra, the dual of the expression is also valid.
- Principle of duality:

$$0 \cdot x = 0 \qquad 1 + x = 1$$

$$1 \cdot x = x \qquad 0 + x = x$$

$$x \cdot x = x \qquad x + x = x$$

$$x \cdot x' = 0 \qquad x + x' = 1$$

The expressions are interchangeable by replacing “0” by “1” and “+” by “ \cdot ”.

Theorem

Idempotent

$$x + x = x$$

$$x \cdot x = x$$

Involution

$$(x')' = x$$

Absorption

$$x + x y = x$$

$$x (x + y) = x$$

Logical adjacency

$$x y + x y' = x$$


DeMorgan

$$\overline{(x + y)} = \bar{x} \bar{y}$$


$$\overline{xy} = \bar{x} + \bar{y}$$

- The complement of sum is equal to the product of the complement
- The complement of product is equal to the sum of the complement

DeMorgan

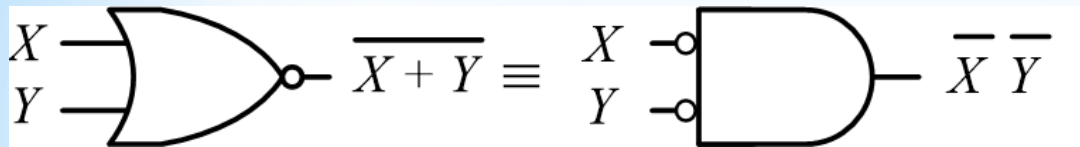

X	Y	$\overline{X + Y}$	$\overline{X} \overline{Y}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

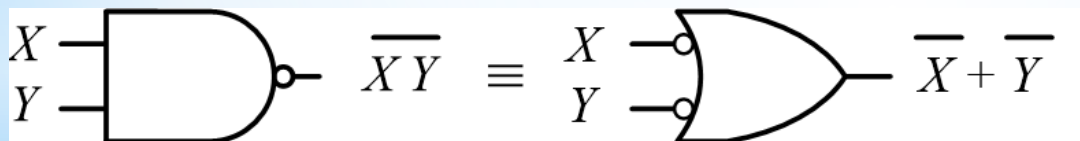


X	Y	$\overline{X Y}$	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Note that $\overline{X + Y} \neq \overline{X} + \overline{Y}$ and $\overline{X Y} \neq \overline{X} \overline{Y}$, a very common mistake !!


3.3 Logic Circuit and Boolean Expression

Boolean expression from a logic circuit

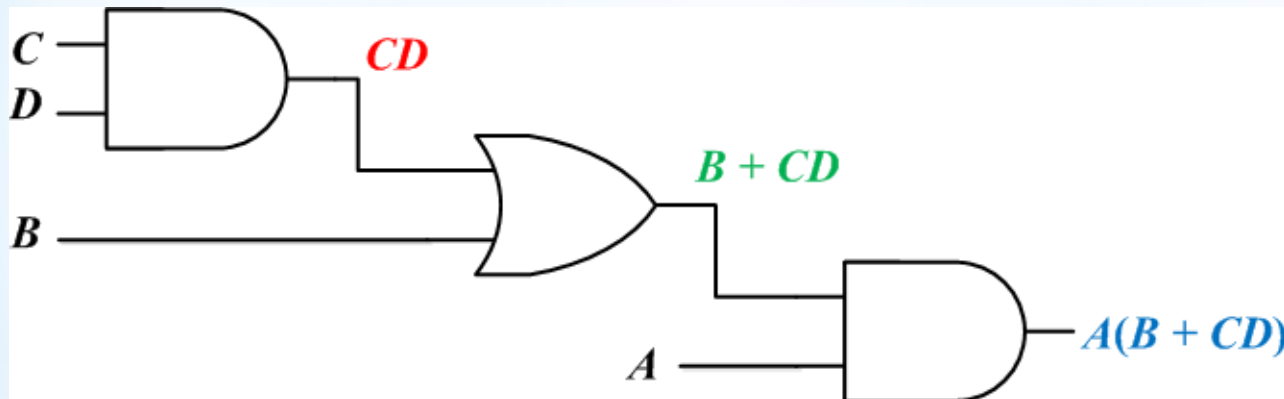

- Write down the output expression from all logic operators
- The Boolean function of this circuit is $A(B + CD)$
- Construct a truth table for above logic circuit

Truth table for a logic circuit

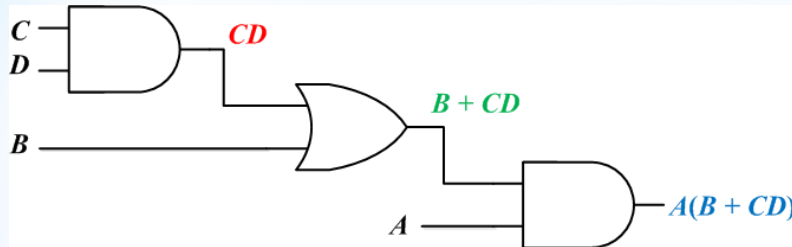

Completed solution for a logic circuit design must include:

1. Boolean Algebra
2. Circuit schematic
3. Truth table


Examples of numbering systems		Inputs				Output
Decimal	Hexadecimal	A	B	C	D	$A(B+CD)$
0	0	0	0	0	0	0
1	1	0	0	0	1	0
2	2	0	0	1	0	0
3	3	0	0	1	1	0
4	4	0	1	0	0	0
5	5	0	1	0	1	0
6	6	0	1	1	0	0
7	7	0	1	1	1	0
8	8	1	0	0	0	0
9	9	1	0	0	1	0
10	A	1	0	1	0	0
11	B	1	0	1	1	1
12	C	1	1	0	0	1
13	D	1	1	0	1	1
14	E	1	1	1	0	1
15	F	1	1	1	1	1

For the truth table, find the output as a following:

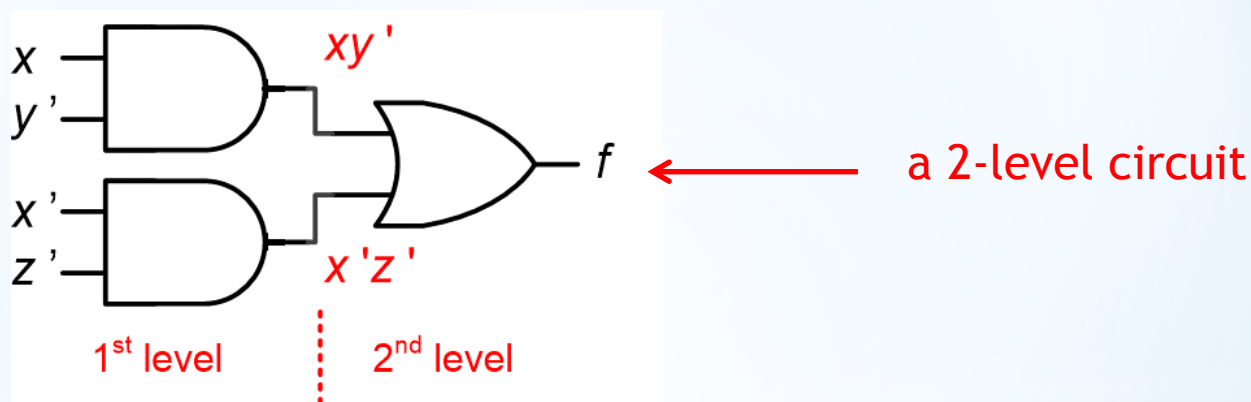
1. Write down all possible input combinations
2. Write down the final stage output (i.e. $A(B + CD)$)

Logic circuit from a Boolean expression

Provided that a Boolean function $f(x,y,z)=xy'+x'z'$, then the logic circuit can be formed as:



or

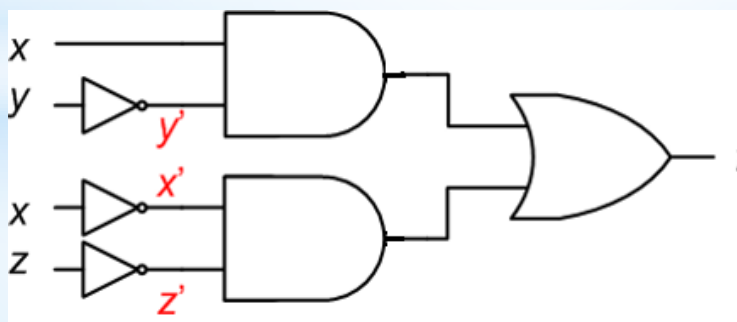

Boolean function → Truth Table

Example: $f(x,y,z)=xy'+x'z'$

Input(s)		Output
x y z	xy' $x'z'$	$xy' + x'z'$
0 0 0	0 1	1
0 0 1	0 0	0
0 1 0	0 1	1
0 1 1	0 0	0
1 0 0	1 0	1
1 0 1	1 0	1
1 1 0	0 0	0
1 1 1	0 0	0

Truth Table → Boolean function

Inputs	Output
<i>a b c</i>	<i>f</i>
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	0
1 1 1	0



f is 1 if $\{(a = 0) \text{ AND } (b = 0) \text{ AND } (c = 1)\}$ OR
 $\{(a = 1) \text{ AND } (b = 0) \text{ AND } (c = 0)\}$ OR
 $\{(a = 1) \text{ AND } (b = 0) \text{ AND } (c = 1)\}$




$$f(a,b,c) = a'b'c + ab'c' + ab'c$$




Is it the simplest form?

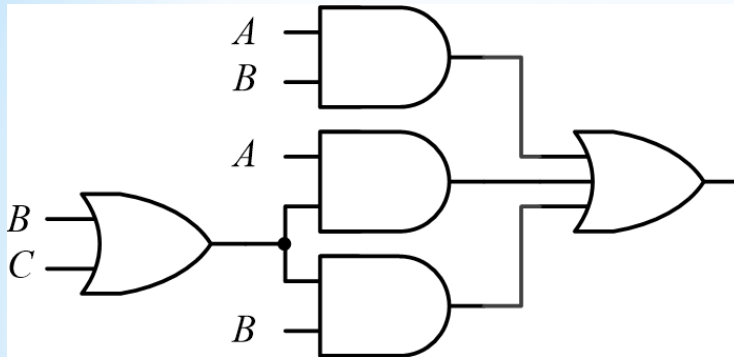Application of Boolean Algebra - simplification



(a)

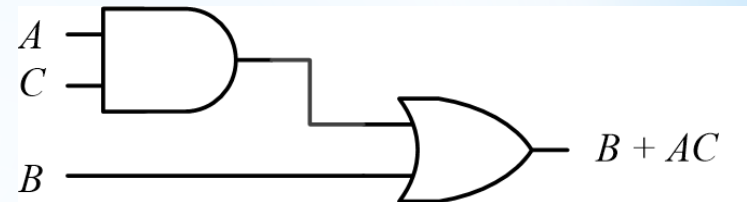

(b)

Prove that the above Circuit (a) is equivalent to Circuit (b).

Solution by Boolean Algebra Simplification

$$\begin{aligned}
 & AB + A(B + C) + B(B + C) \\
 = & AB + AB + AC + BB + BC \\
 = & AB + AB + AC + B + BC \\
 = & AB + AC + B + BC \\
 = & AB + AC + B \\
 = & B + AC
 \end{aligned}$$

$$BB = B$$

$$AB + AB = AB$$

$$B + BC = B$$

$$AB + B = B$$

Idempotent

Idempotent

Absorption

Absorption

3.4 Logic Function - SOP and POS

Logic functions are generally expressed with least number of literals (variables).

- *Sum of products (SOP)*

$$f(a,b,c,d) = ab'c + b'd' + a'cd$$

- *Product of sums (POS)*

$$f(a,b,c,d) = (a' + b + c)(b' + c + d')(a + c')$$

3.4.1 Minterm and Maxterm

Minterm :- For a function of n variables, if a product term contains all n variables **exactly one time** in its complemented or uncomplemented form, the product term is called *minterm*. Complement = 0 and Uncomplement = 1.

Function	Minterm	Not minterm	Not minterm
$f(A, B, C)$	$A' B' C$	$(A B)' C$	$A' B'$ or $AABC$

Maxterm :- If a sum term of a function of n variables contains all n variables **exactly one time** in its complemented or uncomplemented form, the sum term is called a *maxterm*. Complement = 1 and Uncomplement = 0.

Function	Maxterm	Not maxterm	Not maxterm
$f(A, B, C)$	$A' + B' + C$	$(A + B)' C$	$A' + B'$ or $A' + B + B + C$

Noted that the minterm and maxterm cannot be simplified.

Minterms and maxterms for 3 variables logic function

			Minterms		Maxterms	
x	y	z	Term	designation	term	designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

The number of minterms and maxterm of a logic function of n variables equals to 2^n , e.g. $f(a,b,c,d) \rightarrow 16$ minterms (maxterms);

$f(a,b,c,d,e) \rightarrow 32$ minterms (maxterms).

3.4.2 Canonical form

The canonical form of a logic function is a presentation in either minterms or maxterms.

In minterm form (with logic output “1”):

$$f(A, B, C) = \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}BC + ABC$$

Minterm	Code	Number
$A'BC'$	010	m_2
ABC'	110	m_6
$A'BC$	011	m_3
ABC	111	m_7

$$f(A, B, C) = m_2 + m_3 + m_6 + m_7$$

Canonical form $f(A, B, C) = \sum m(2, 3, 6, 7)$

Noted for minterm: Complement = 0 and Uncomplement = 1

The canonical form of a logic function is a presentation in either minterms or maxterms.

In maxterm form (with logic output “0”):

$$f(A, B, C) = (A + B + C)(A + B + \bar{C})(\bar{A} + B + C)(\bar{A} + B + \bar{C})$$

Maxterm	Code	Number
$A + B + C$	000	M_0
$A + B + C'$	001	M_1
$A' + B + C$	100	M_4
$A' + B + C'$	101	M_5

$$f(A, B, C) = M_0 M_1 M_4 M_5$$

Canonical form $f(A, B, C) = \prod M(0, 1, 4, 5)$

Noted for maxterm: Complement = 1 and Uncomplement = 0

Canonical SOP representation:

$$\begin{aligned}f(a,b,c) &= a + \bar{b}c \\&= a(b + \bar{b}) + \bar{b}c(a + \bar{a}) \\&= ab(c + \bar{c}) + a\bar{b}(c + \bar{c}) + \bar{b}c(a + \bar{a}) \\&= abc + ab\bar{c} + a\bar{b}c + a\bar{b}\bar{c} + \bar{a}bc + \bar{a}\bar{b}c \\&= m_1 + m_4 + m_5 + m_6 + m_7 \\f(a,b,c) &= \sum m(1,4,5,6,7)\end{aligned}$$

Canonical POS representation:

$$\begin{aligned}
 f(x, y, z) &= xy + \bar{x}z \\
 &= (xy + \bar{x})(xy + z) = (x + \bar{x})(y + \bar{x})(x + z)(y + z) \\
 &= (\bar{x} + y)(x + z)(y + z) = (\bar{x} + y + z\bar{z})(x + z + y\bar{y})(y + z + x\bar{x}) \\
 &= (\bar{x} + y + z)(\bar{x} + y + \bar{z})(x + z + y)(x + \bar{y} + z)(x + y + z)(\bar{x} + y + z) \\
 &= (x + y + z)(x + \bar{y} + z)(\bar{x} + y + z)(\bar{x} + y + \bar{z})
 \end{aligned}$$

$$f(x, y, z) = M_0 M_2 M_4 M_5 = \Pi M(0, 2, 4, 5)$$

Conversion between canonical forms

Relationship

$$\overline{\text{maxterm}_i} = \text{minterm}_i \text{ (i.e. } \overline{M_i} = m_i)$$

$$\overline{\text{minterm}_i} = \text{maxterm}_i \text{ (i.e. } \overline{m_i} = M_i)$$

$$\begin{aligned} \text{e.g. } M_3' &= (a + b' + c') \\ &= a'bc \text{ (De Morgan's Theorem)} \\ &= m_3 \end{aligned}$$

Canonical form conversion: SOP \leftrightarrow POS

For minterm representation (**choose all the terms with output 1**):

$$f(x, y, z) = \bar{x} \bar{y} z + x \bar{y} \bar{z} + x \bar{y} z + x y z$$

$$f(x, y, z) = m_1 + m_4 + m_5 + m_7 = \sum m(1, 4, 5, 7)$$

For maxterm representation (**choose all the terms with output 0**):

$$\overline{f(x, y, z)} = \bar{x} \bar{y} \bar{z} + \bar{x} y \bar{z} + x \bar{y} \bar{z} + x y \bar{z}$$

$$\begin{aligned} f(x, y, z) &= \overline{\bar{x} \bar{y} \bar{z} + \bar{x} y \bar{z} + x \bar{y} \bar{z} + x y \bar{z}} \\ &= (x + y + z)(x + \bar{y} + z)(x + \bar{y} + \bar{z})(\bar{x} + \bar{y} + z) \end{aligned}$$


$$f(x, y, z) = M_0 M_2 M_3 M_6 = \prod M(0, 2, 3, 6)$$

$x \ y \ z$	f
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	0
1 1 1	1


Noted that for maxterm the uncomplemented variable = 0,
complemented variable = 1

3.5 Synthesis of logic function

$$f(a,b,c) = \bar{a}b + a\bar{c}$$



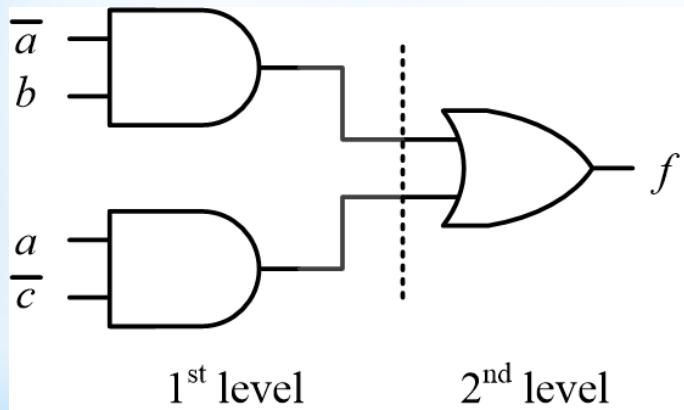


$$f(a,b,c) = (a+b)(\bar{a}+\bar{c})$$



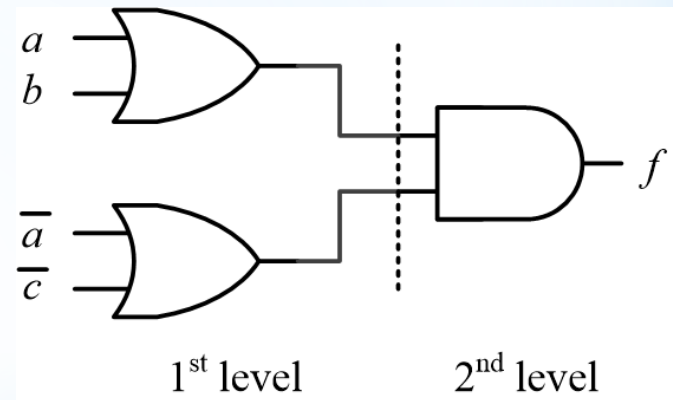


3.6 Structure of one gate type

Universal gate: NAND gate

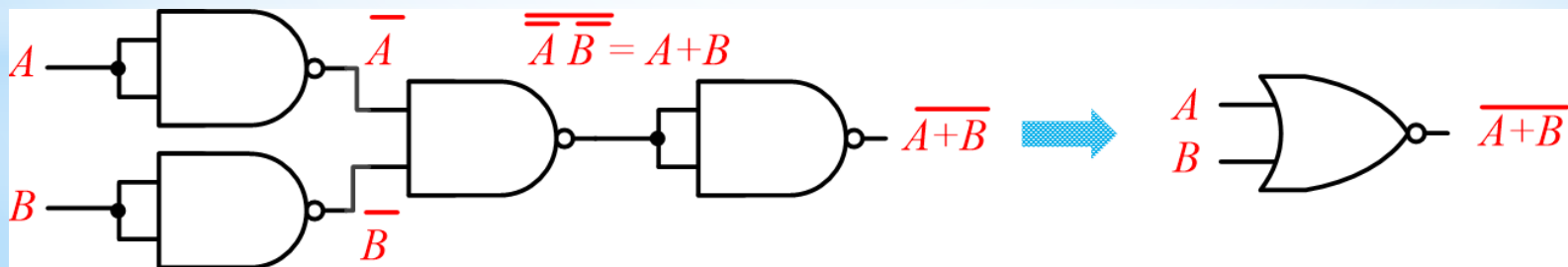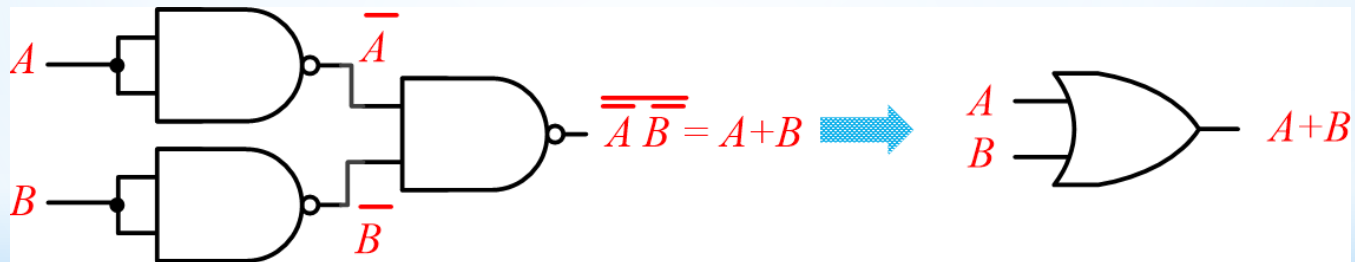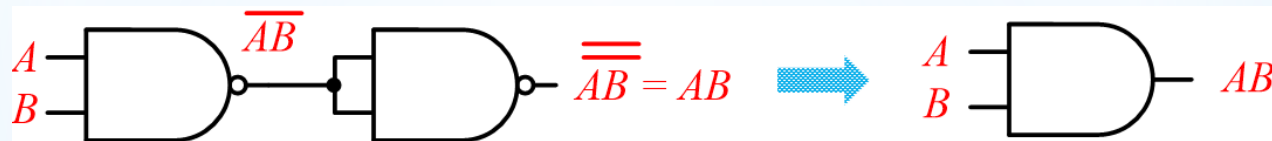


Universal gate: NOR gate

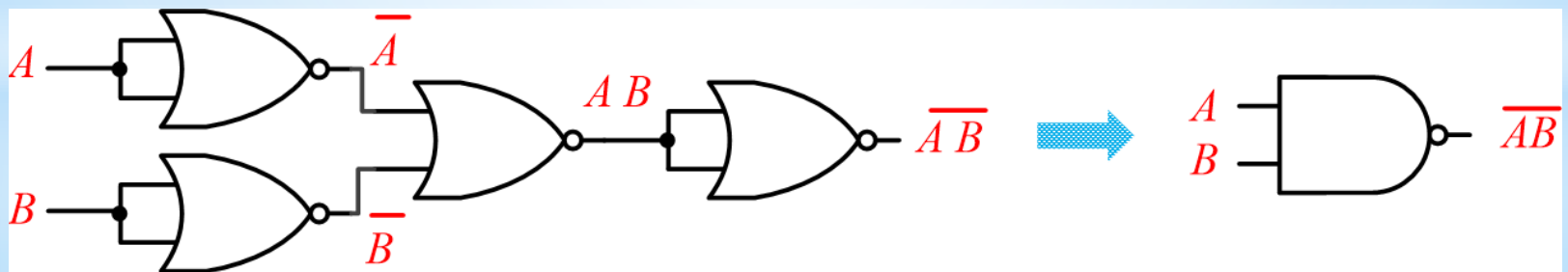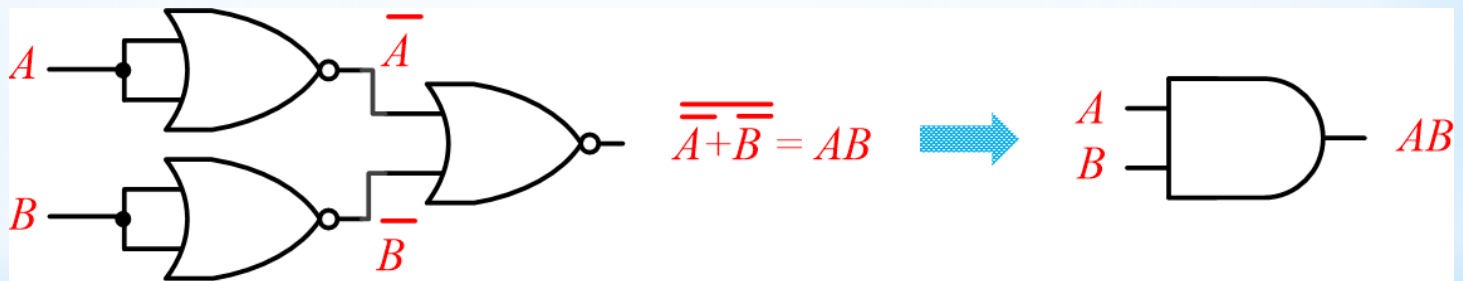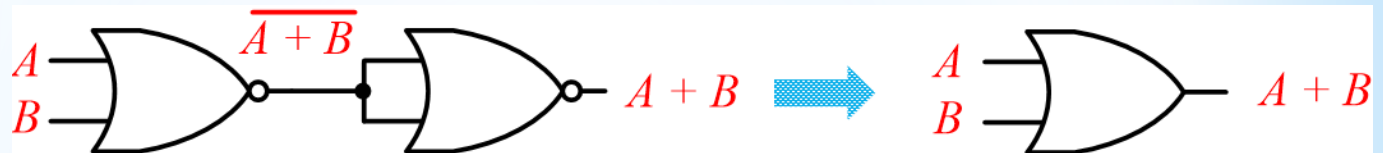

NAND implementation

Modify the Boolean function to get rid of the “OR” operation
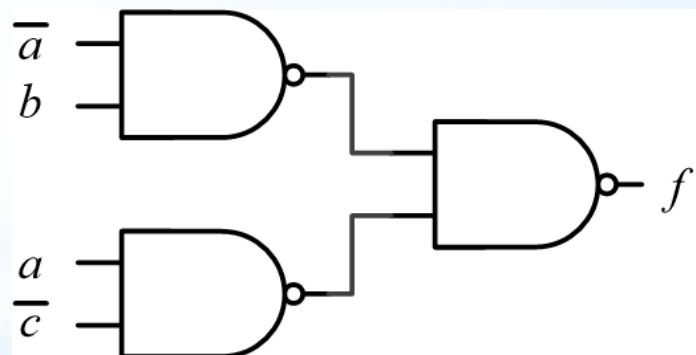
$$\begin{aligned} f(a, b, c) &= \overline{a}b + a\overline{c} \\ &= \overline{\overline{\overline{a}b} + \overline{a\overline{c}}} \\ &= \overline{\overline{a}b} \overline{a\overline{c}} \end{aligned}$$




Note inverter can be implemented using NAND gate.

NOR implementation

Modify the Boolean function to get rid of the “AND” operation
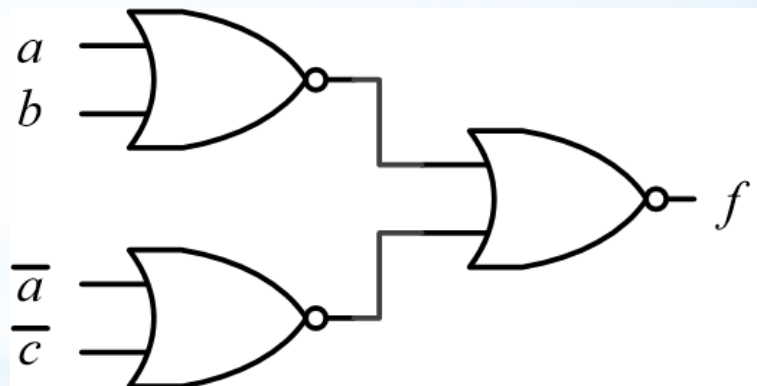
$$\begin{aligned} f(a, b, c) &= (a + b)(\bar{a} + \bar{c}) \\ &= \overline{\overline{(a + b)(\bar{a} + \bar{c})}} \\ &= \overline{\overline{a + b} \cdot \overline{\bar{a} + \bar{c}}} \\ &= \overline{\overline{a + b}} + \overline{\overline{\bar{a} + \bar{c}}} \\ &= a + b + a + c \end{aligned}$$



Note inverter can be implemented using NOR gate.